

Do-It-Yourself Diodes

Society for Amateur Scientists
National Citizen Science Conference
August 2006

Ed Nisley - KE4ZNU
ed.nisley@ieee.org

Coming Attractions

Radio Rocks

EZ Curve Tracer

Radio Circuit Model

Mineral Diodes & Thingies

Rust Never Sleeps

Why Diodes Matter


In The Beginning

- Before integrated circuits...
- Before transistors...
- Before vacuum tubes...
- Before *electronics*...
- ... there were radios!
 - Modern radio by VE6AB



The Simplest Possible Radio

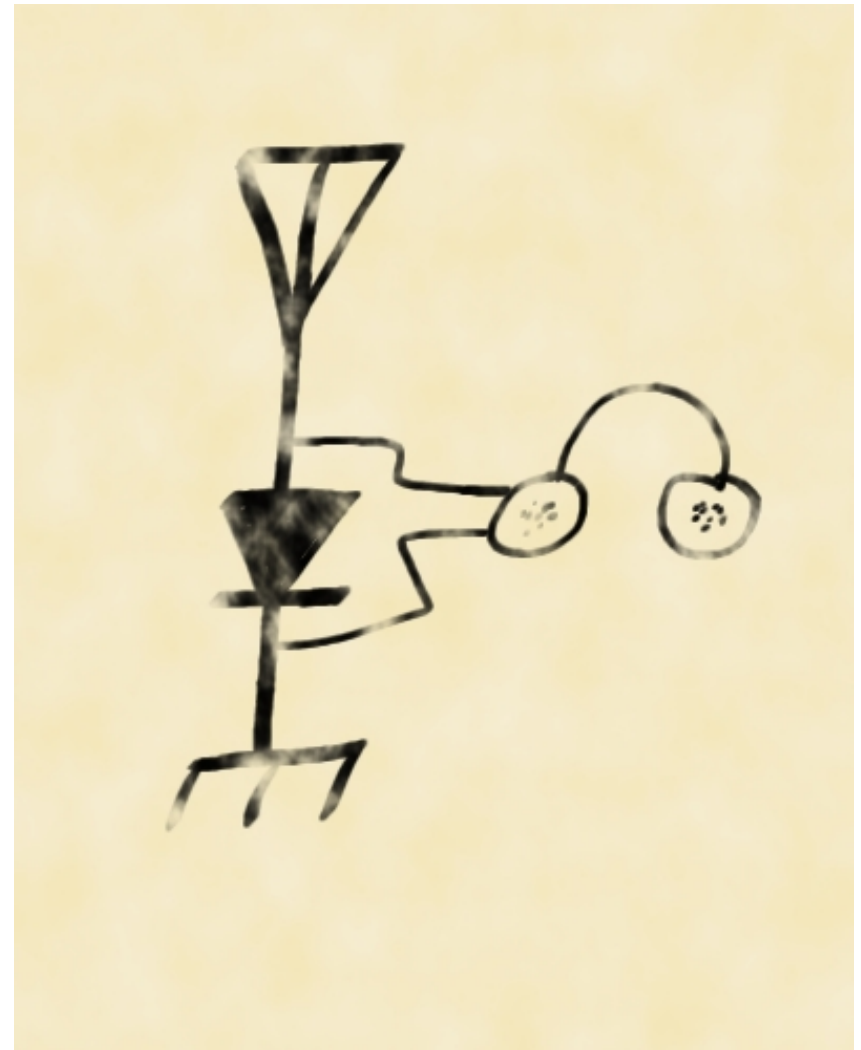- Antenna
- Ground
- Earphone
- Detector
 - AM demodulator (huh?)
 - A rock on a hard place
 - Crystal diode!
- Tuning? Hah!




Mineral Samples

- Who knew?
 - Nobody!
 - Conflicting stories
- Try all combinations
 - Most don't work at all
 - How can you tell?
- Instrumentation!




The Big Idea

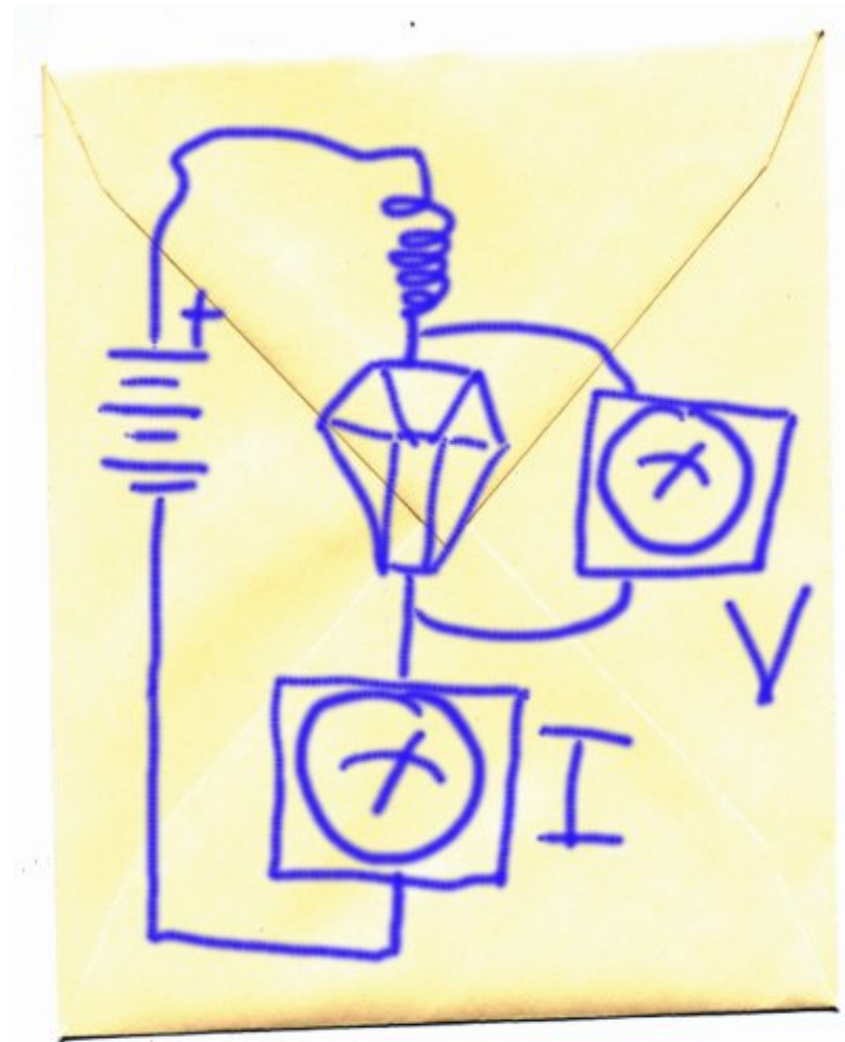- Jam current (I) in
 - How much?
 - Polarity?
- Measure volts (V) across
 - Range?
- Plot results: curves!
 - It can be done manually
 - More fun automatically
 - Oscilloscope screen shots




The Little Details

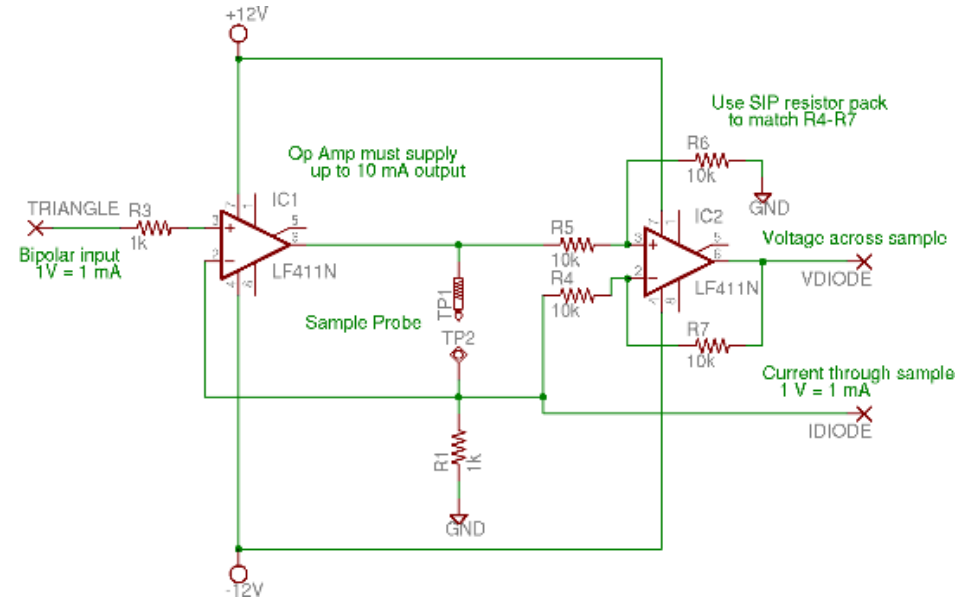- Triangle wave input
 - 200 Hz, 8 V peak
 - Voltage to Current
 - Oscilloscope X axis
- Measure V at sample
 - Differential to single
 - Oscilloscope Y axis
- ± 10 mA and ± 10 V
 - Still makes sparks...



Enlarged to Show Texture

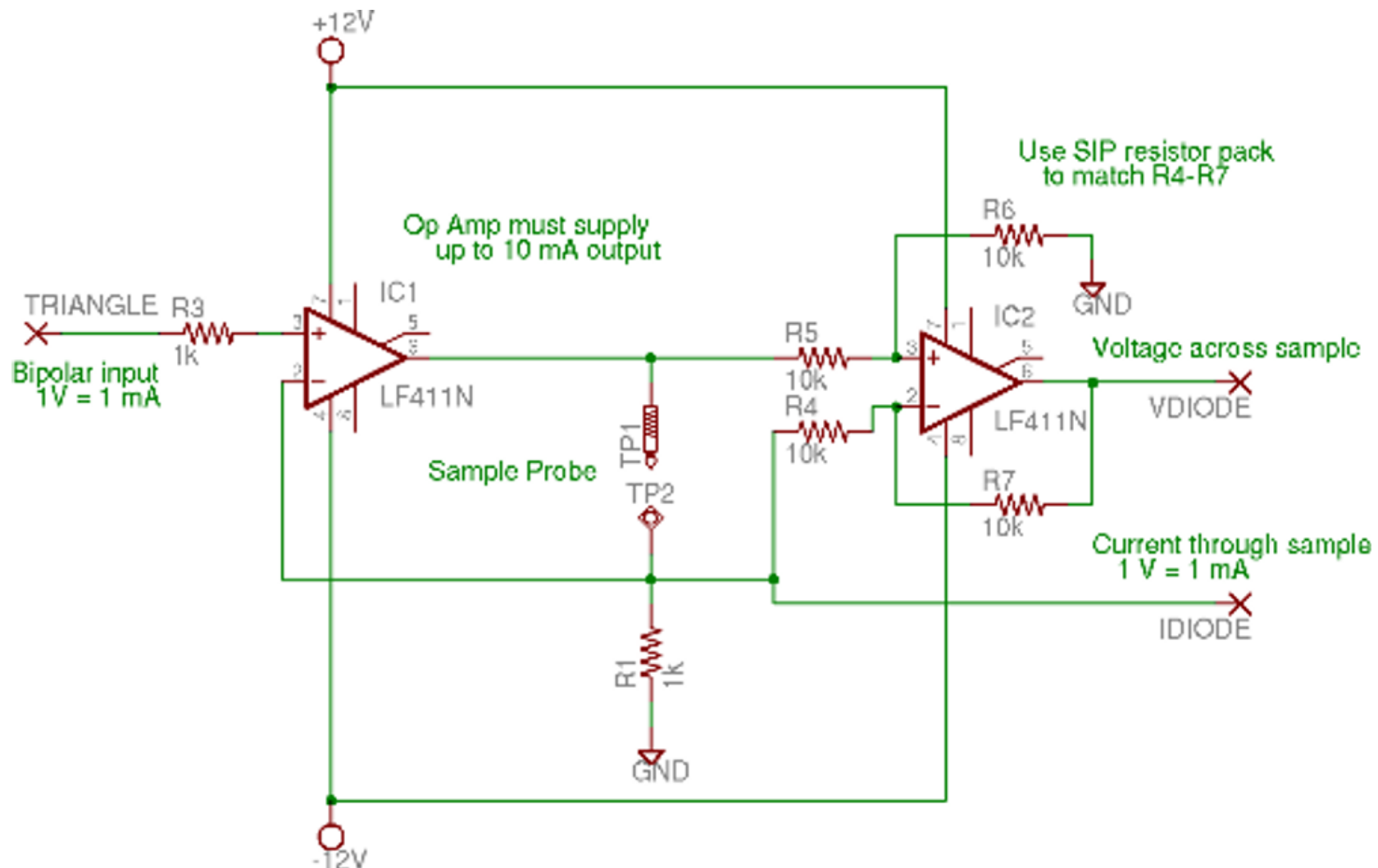


Cat's Whisker Probe

- Mineral in metal pot
- Wire pin-point probe
 - Steel? Bronze? Carbon?
- 3-axis ball slide mount
- Springy thing
- Patience



He Who Dies With The Most Stuff...

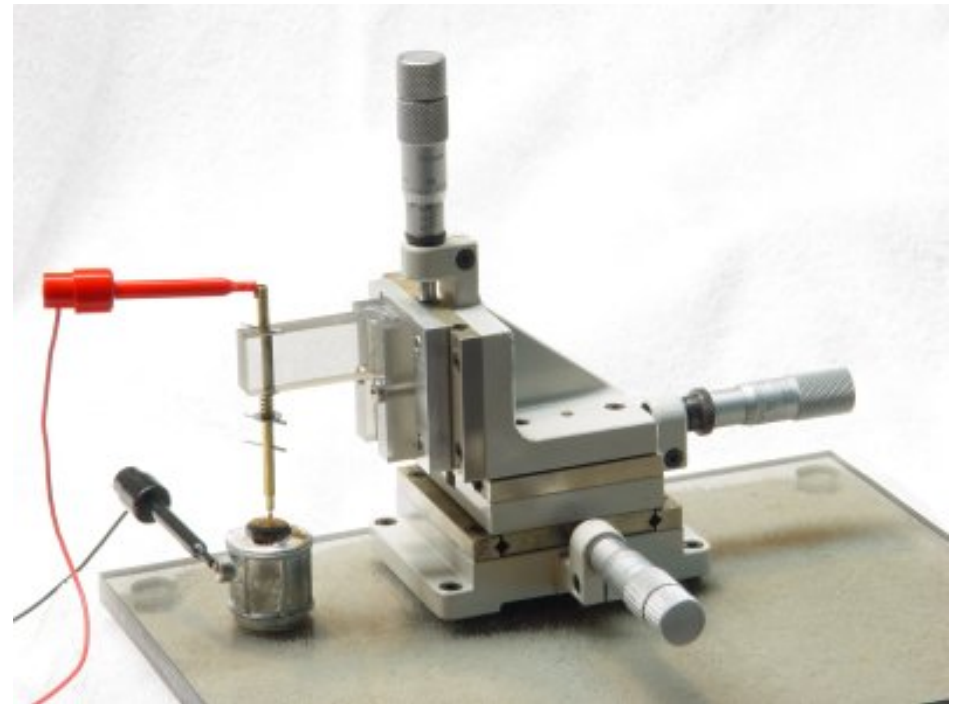- 3-axis positioner
 - 0.001" resolution
 - 0.5" accessible cube
 - Zero backlash
- Black-belt dweebdom



Probe and Sample Holder

- Telescoping brass tubes
- Tapered clock pins
- Springy thing
- EMT fitting
- Gratuitous CNC
- Low frequency = clips




Sample Holder

- Wood's Metal
 - Makes solid contact
 - But: **Pb+Cd+Bi+Sn**
 - But: melts at 160° F
 - Use Field's Metal?
- Friction-fit probe tips
 - Steel, bronze, carbon
 - Small differences?




Calibration – 1 k Ω Resistor

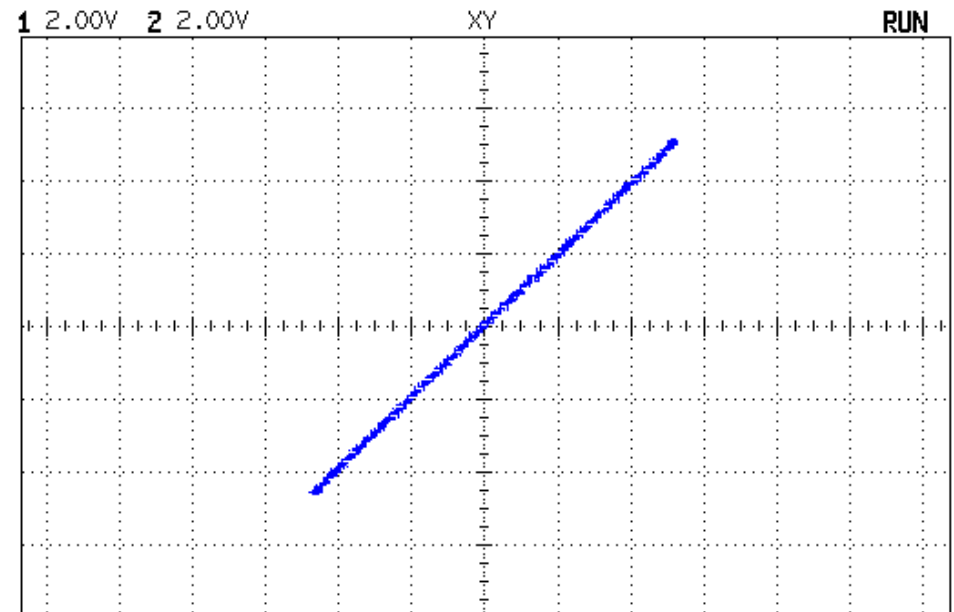- 1 V input = 1 mA
- Scope Axes
 - X = current (2 mA/div)
 - Y = voltage (2 V/div)
- Linear!
 - Whew...
- Set DC offset = 0




Calibration – 1N914

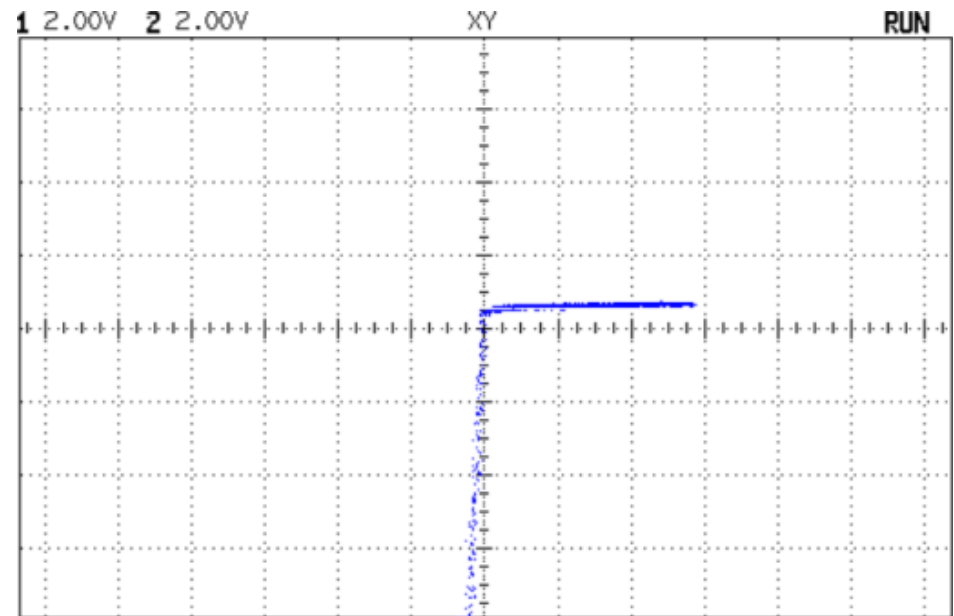- Jellybean Si diode
- $V_{\text{fwd}} = 0.5 \text{ V}$
 - Pretty close
- $I_{\text{rev}} = \text{zilch}$
 - Limited by diff amp's input resistance




Iron Pyrite

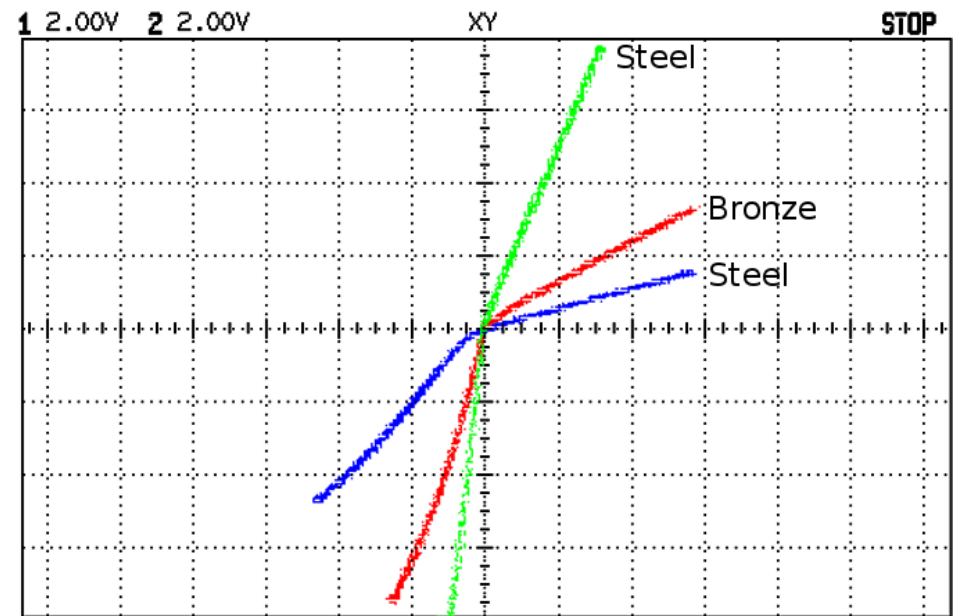- Green trace
 - Nearly a resistor
- Red trace
 - More like a diode
- Blue trace
 - Both better & worse
- Same lump!
- Probe material?




Spice Circuit Model

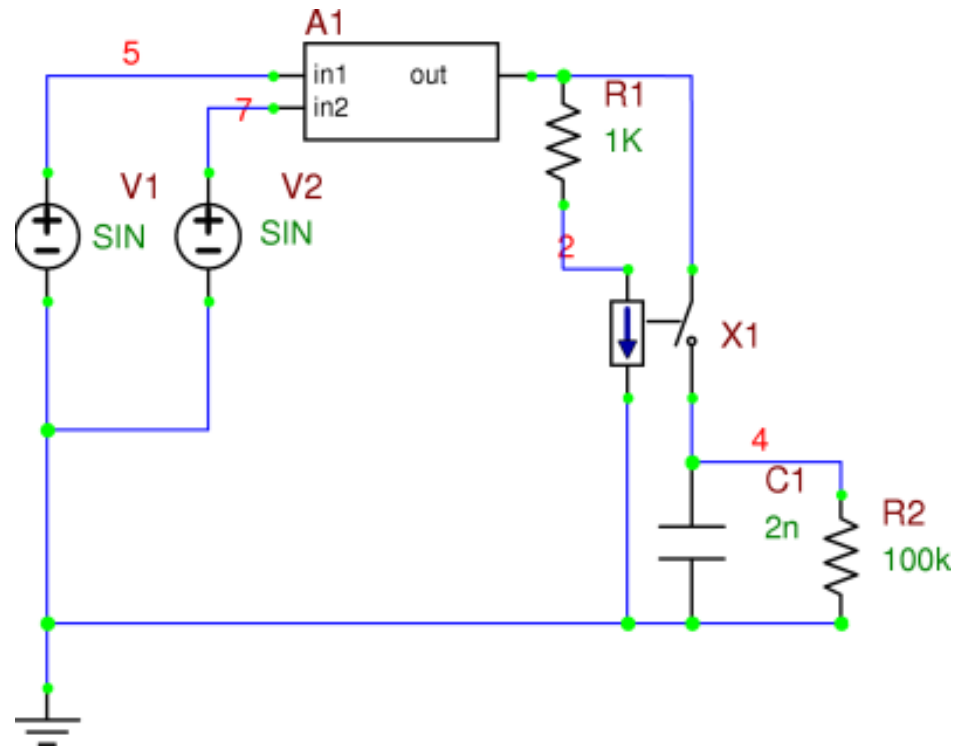- Diode = switch
 - Voltage controlled
 - Maybe a lousy switch
- Resistance from plots
 - $R = \Delta V / \Delta I = \text{slope}$
- C1 & R2 \approx earphone
 - High impedance
- $V1 * V2 = \text{AM signal!}$




AM Demodulation

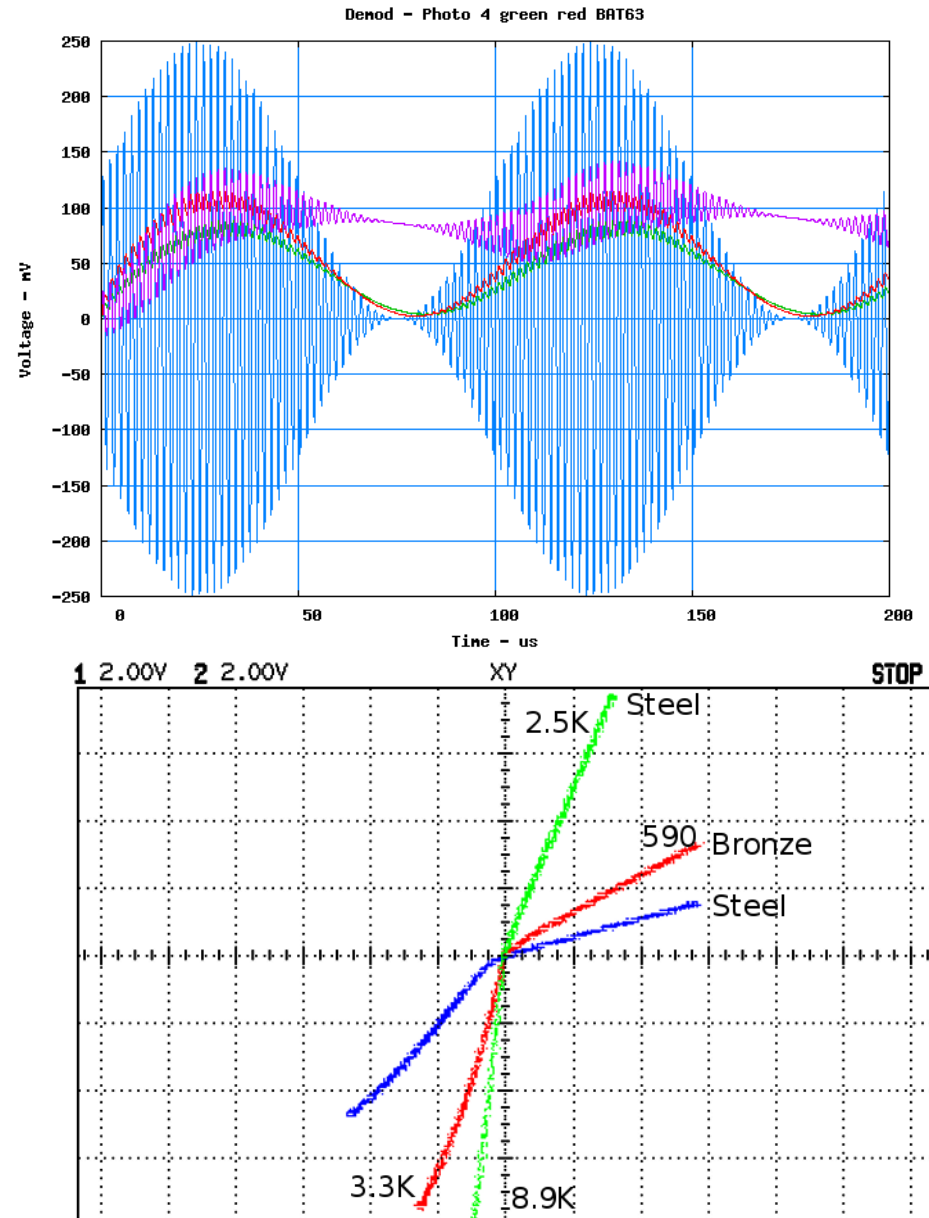- Low voltage RF
 - This is before tubes!
- Poor diodes are OK
 - Green $\approx 3.6 / 1$ (rev/fwd)
 - Red $\approx 5.6 / 1$
- Modern diodes are NG
 - Purple = Schottky $\approx \infty / 1$
 - But V_{fwd} still too high




Iron Pyrite

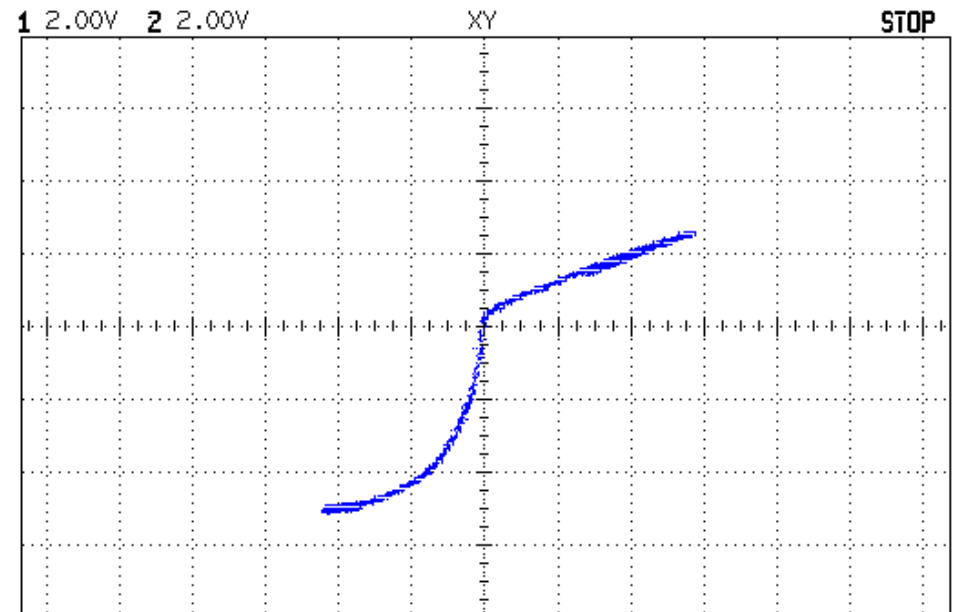- Huh?
 - Sorta Zener-ish
- Marginal diode
 - For low I & V, anyway




Lead - Galena?

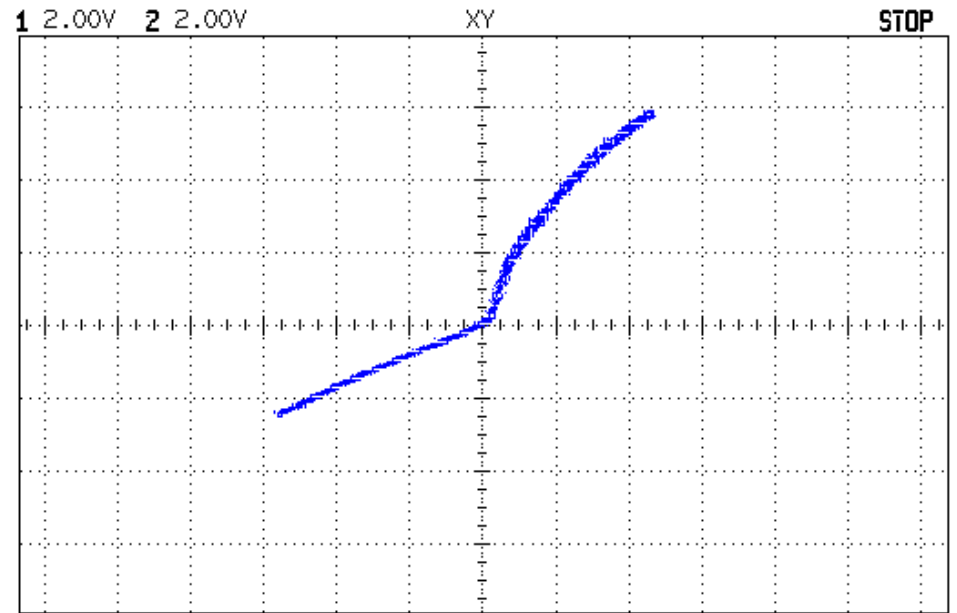- Backwards polarity
 - Whatever that means
- Low V_{fwd}
- Bronze probe
- Best of a bad sample
 - Who knew?
 - Maybe it's just lead?




Chalcopyrite

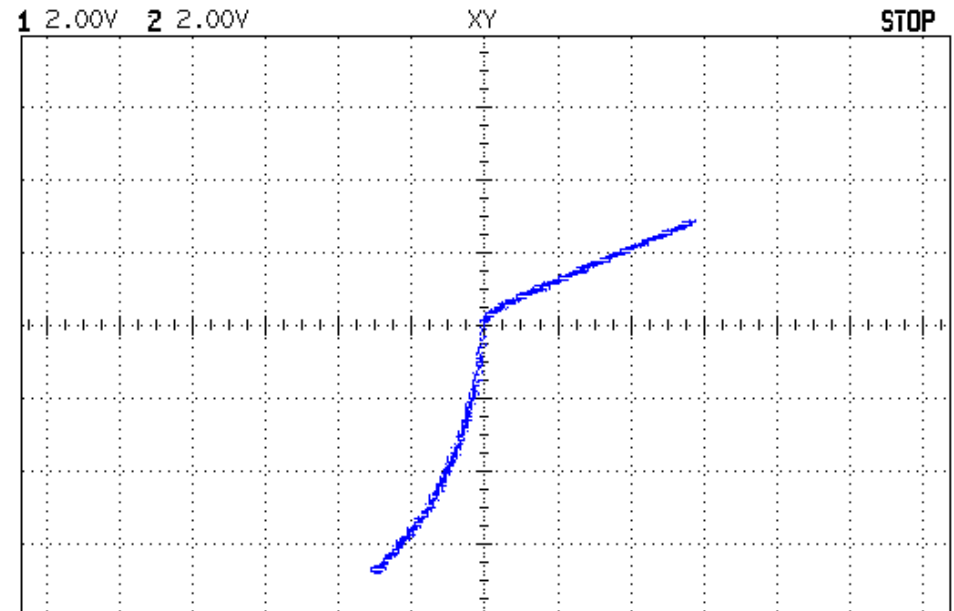- Say kal'•keh•pie'•right
- Looks diode-ish
 - If you squint
- Low V_{fwd}
- But wait...




Chalcopyrite

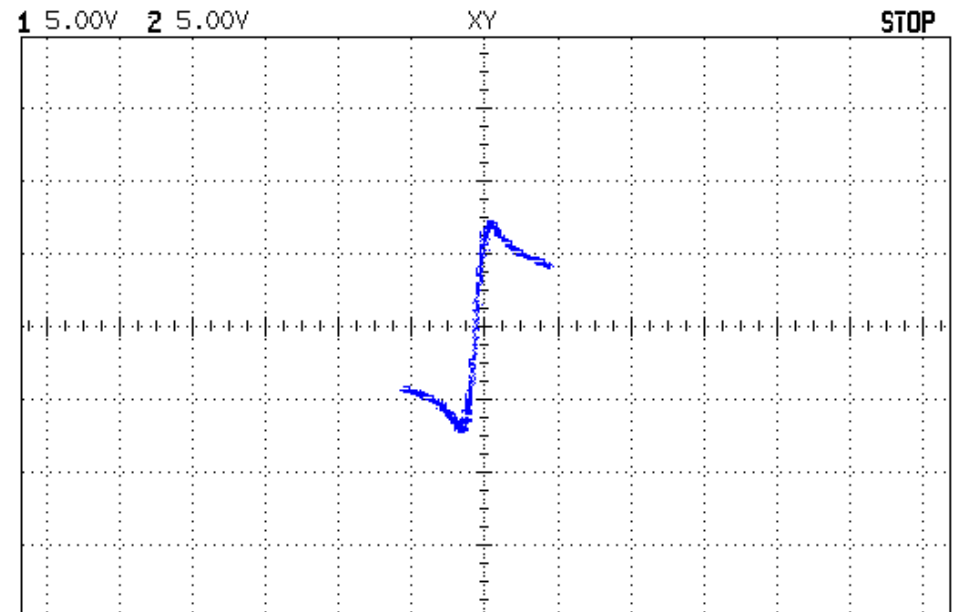- It's a Diac!
 - Bilateral trigger diode
- It's a resistor!
 - For *very* low I
- Negative resistance
 - Current \uparrow = Voltage \downarrow
- Note scale change
 - 5 V and 5 mA / div







Galvanized Steel

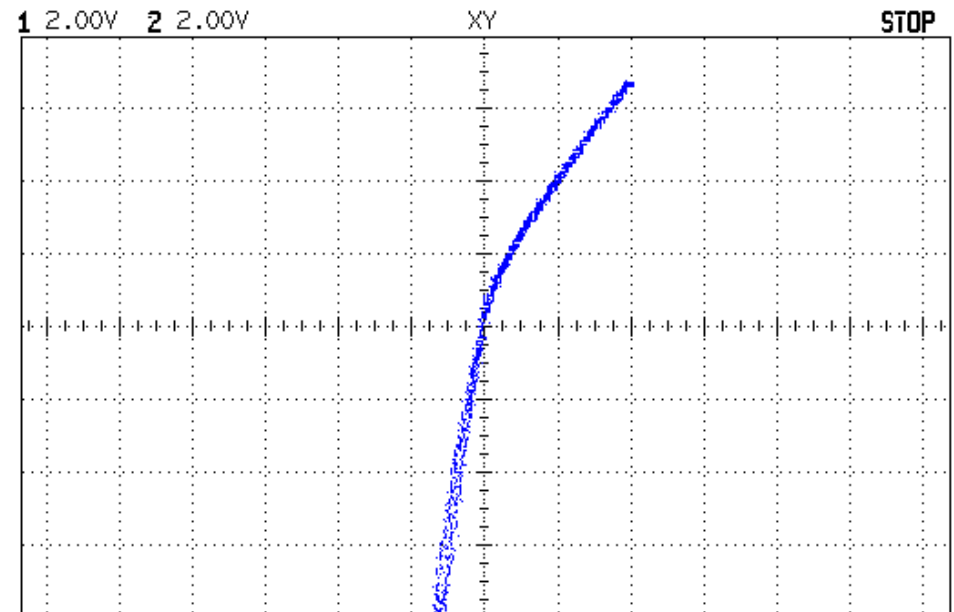- Propane torch
 - Little black spots...
 - Do this outdoors!
- Iron-tin-zinc alloy?
 - Cadmium? *Ick!*
- Looks like high R
 - And not a diode
- But wait...



Galvanized Steel Bestiary

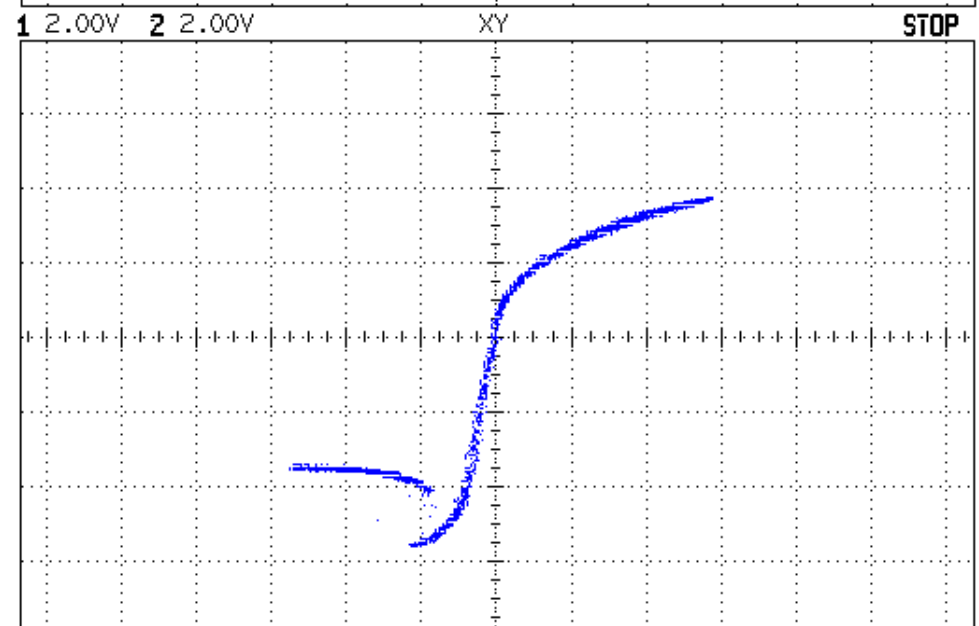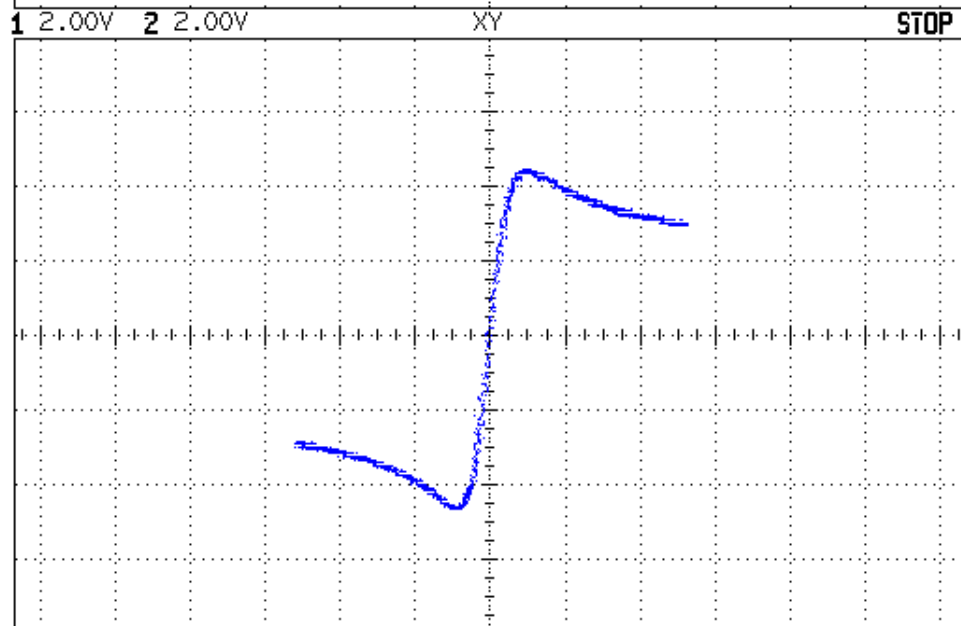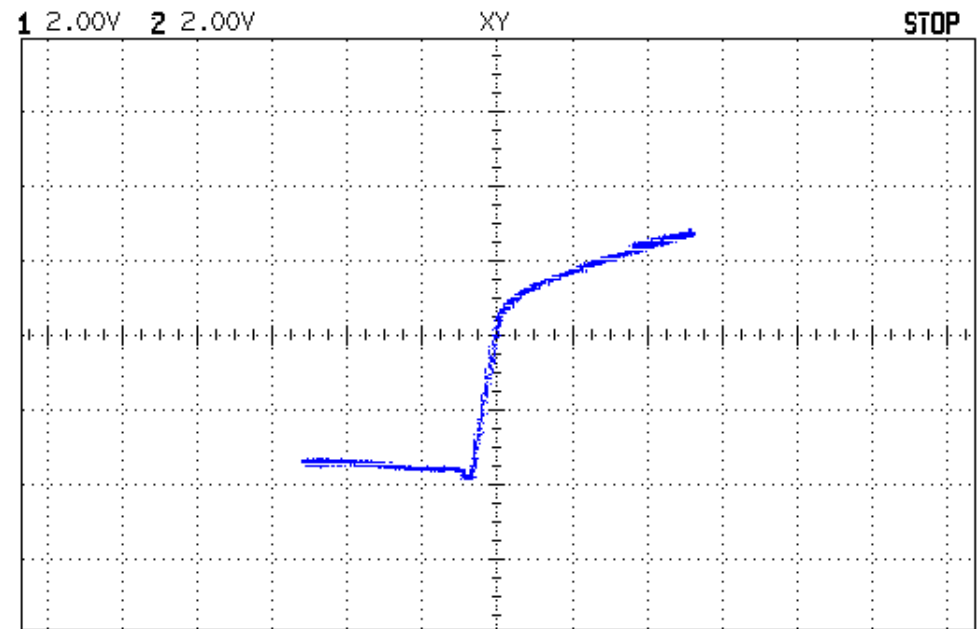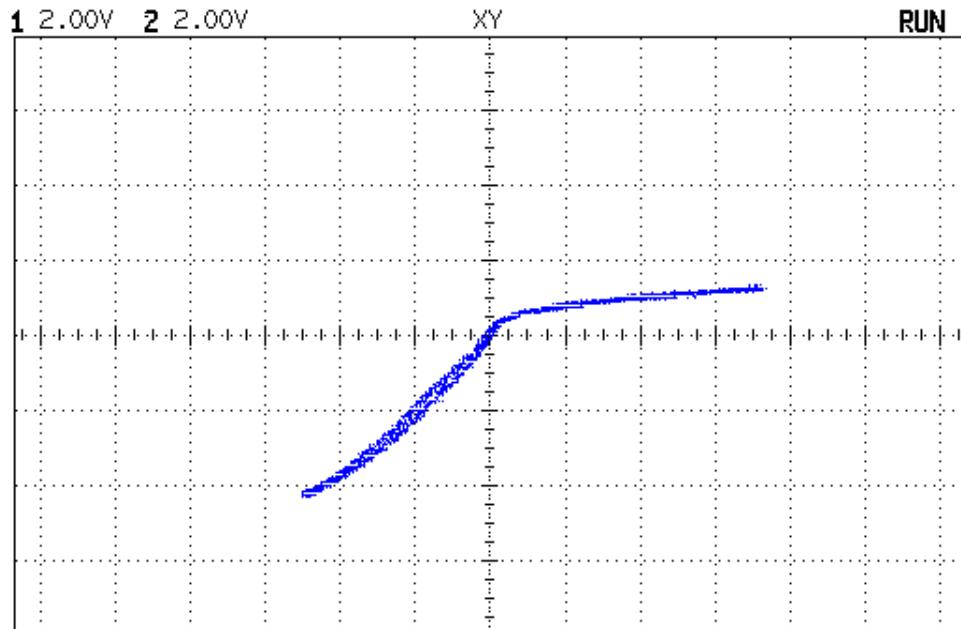


Rust Never Sleeps

- Ordinary steel bolt
- Salt + towel + copper
 - $\text{Cu} + \text{Fe} = 650 \text{ mV}$
 - At *only* 1 mA
 - Slow and steady
- AA cell
 - 1500 mV & 10 mA
 - 4 hours later...




Steel Corrosion

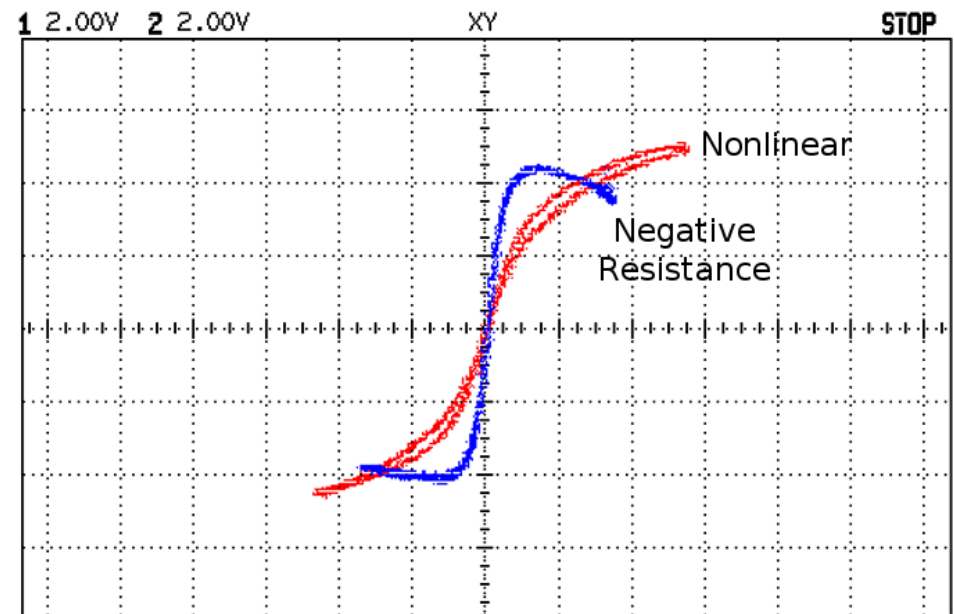- Nonlinear
- Symmetric
 - Sorta, kinda
- Negative resistance
 - Oscillator!
- No Battery Needed
 - Self-biasing circuitry
 - DC bias + small AC




Linear Mixing Circuit

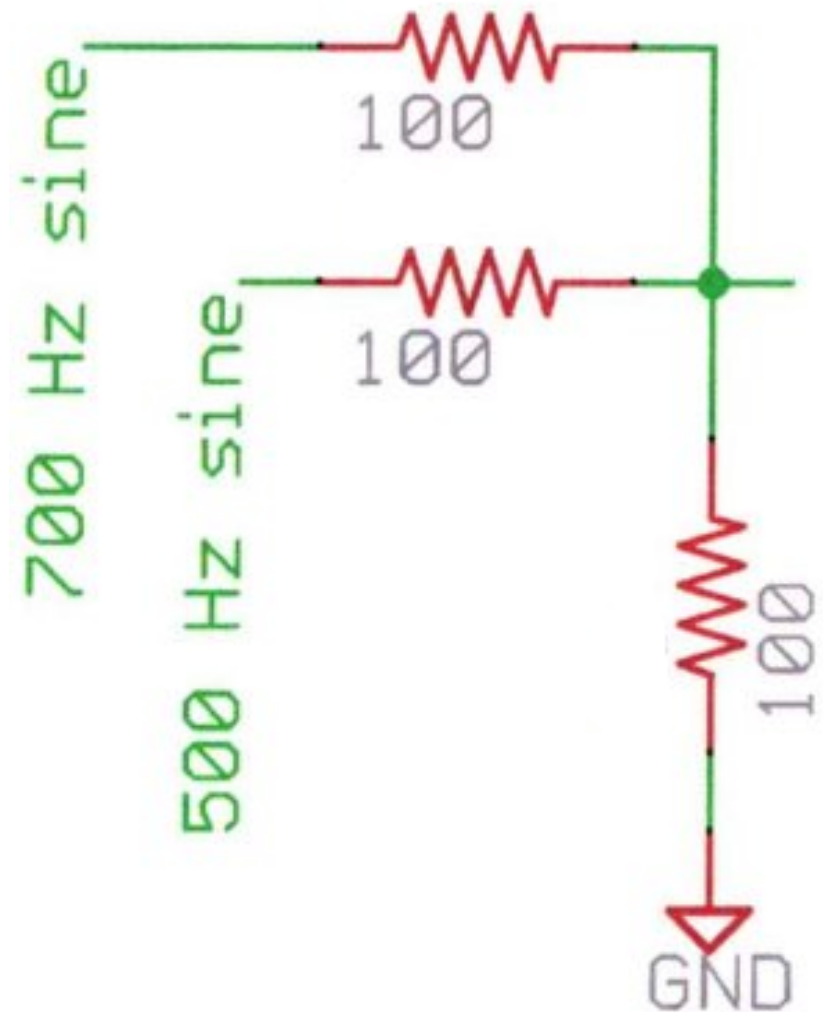- Linear mixing
 - Only “resistors”
 - Sum of amplitudes
 - No surprises
 - Ohm’s Law, etc




Linear Mixing Results

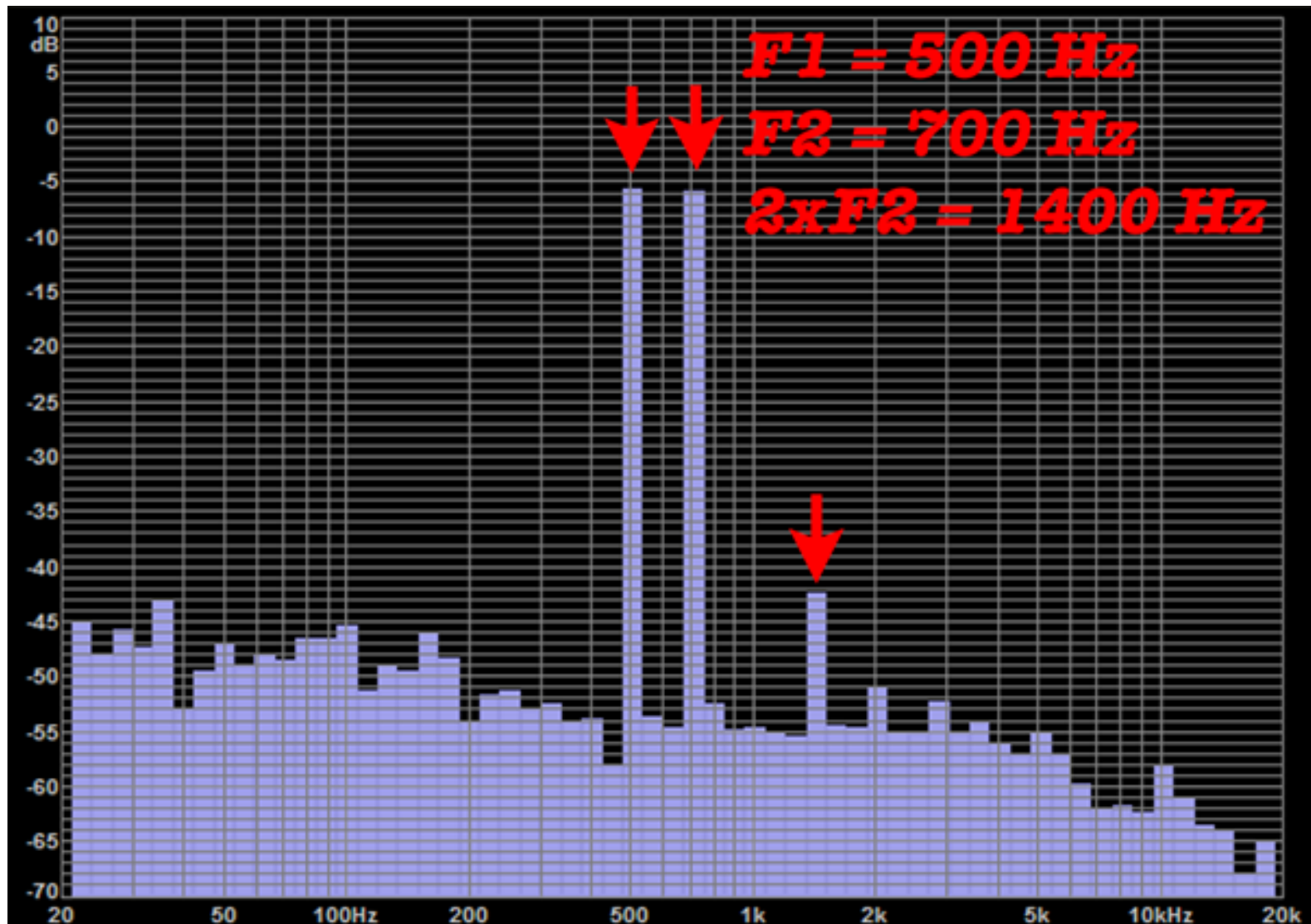


Nonlinear Mixing Circuit

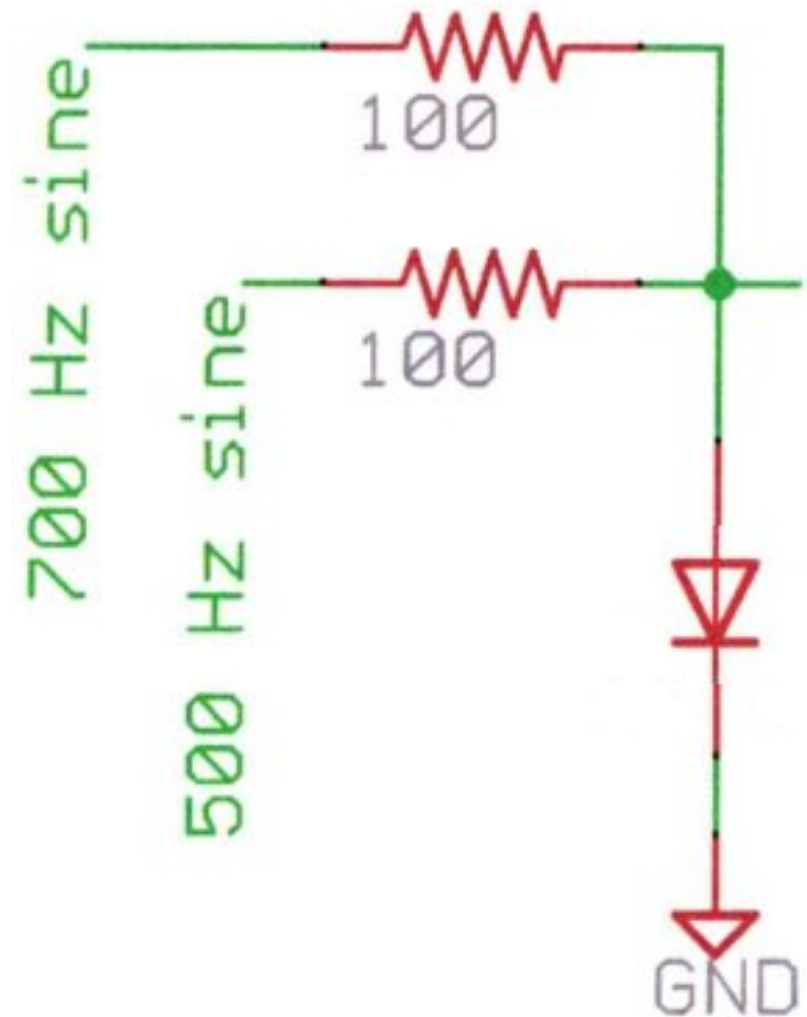- Nonlinear mixing
 - Usually a diode, but ...
 - *Any* nonlinearity will do
 - $\pm nF_1 \pm mF_2$
 - Amplitudes? Hah!
 - No analytic equations
 - Simulation values?



Nonlinear Mixing Result

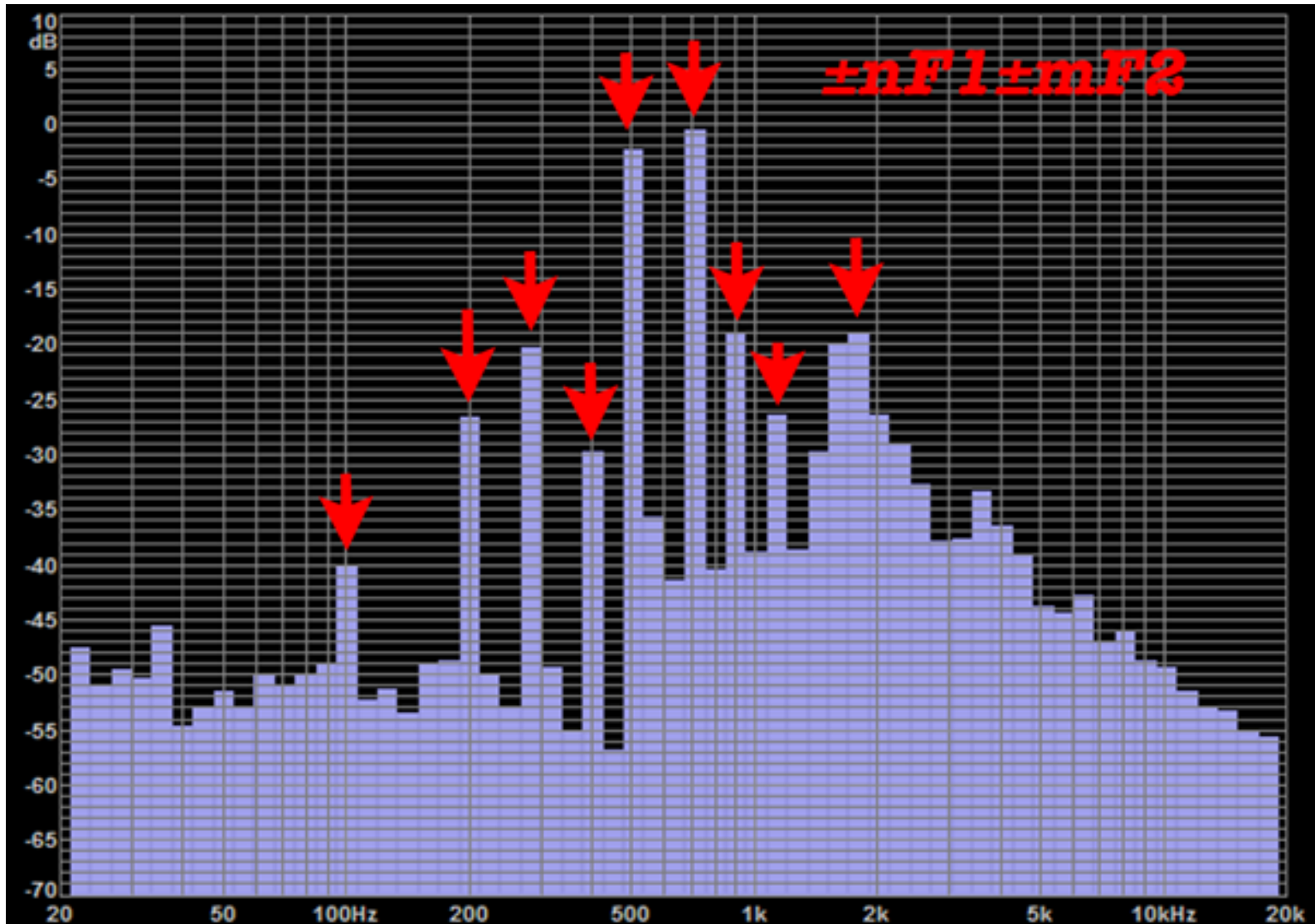

RF vs. The Rusty Bolt


- Mountaintop radio
 - *Many* transmitters
 - High RF field intensity
 - Sensitive receivers
 - Galvanized towers
 - Acid rain
- Corrosion
- Intermodulation!
 - $\pm nF_1 \pm mF_2 \pm pF_3 \pm \dots$



Mt Beacon NY - Photo by WB2UWU

DIY Diodes

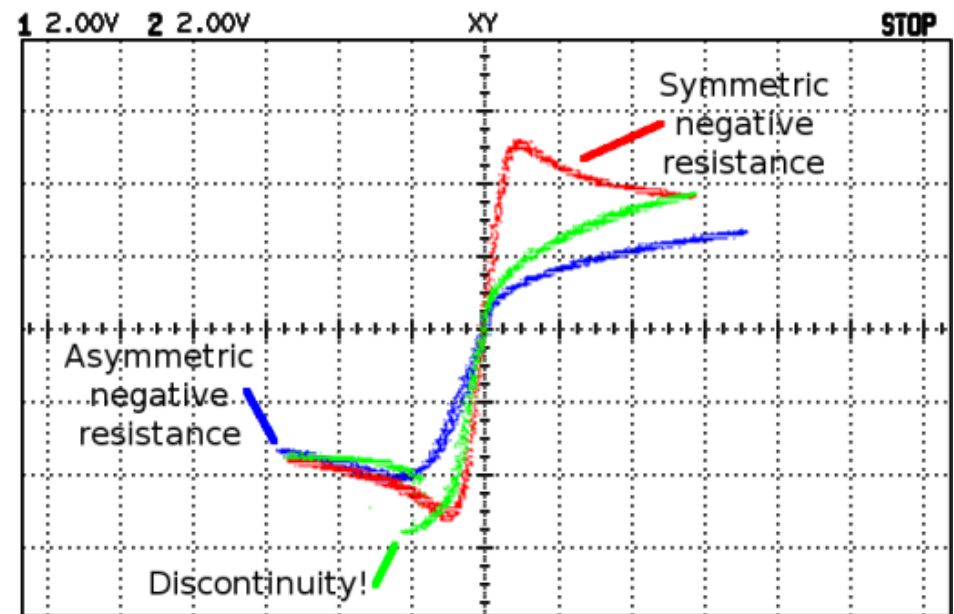- They're everywhere
- They're cheap
 - OK, not that positioner
- They're easy, sorta
- You'll learn...
 - ... about electronics
 - ... about patience
- ***Demo: Sunday AM!!***



References

My column in Circuit Cellar magazine: www.circuitcellar.com

October 2006 is mostly this talk, has file of scripts, pictures, other stuff

February & April 2003 describe nonlinear frequency mixing

Semiconductor curve tracer using PC sound card: George Steber, WB9LVI

Circuit Cellar, Jan 2004

ARRL QEX, July 2006: <http://www.arrl.org/qex/2006/07/qx7steber.pdf>

Good overview of crystal-set parameters: <http://www.olderadioworld.de/gollum/analysis.htm>

Zinc negative resistance oscillators: <http://home.earthlink.net/~lenyr/zincosc.htm>

Galvanic Series table: <http://www.ocean.udel.edu/seagrants/publications/corrosion.html>

Wood's metal, springs, phosphor bronze sheet, tools from MicroMark: <http://micromark.com/>


Taper pins and small parts from S. LaRose, Inc: <http://www.slarose.com/> (dead on 18 Aug 06)

Capturing oscilloscope traces with Kermit: <http://www.columbia.edu/kermit/index.html>

Converting HPGL to bitmaps with hp2xx utility: <http://www.gnu.org/software/hp2xx/>

Who Am I?

- Ed Nisley
 - Say “NISS-lee”, even though my ancestors were half-essed
 - Engineer, author, tinker, family guy
 - Circuit Cellar: Above the Ground Plane - www.circuitcellar.com
 - Analog & RF stuff
 - Dr Dobb's Journal: Nisley's Notebook - www.ddj.com
 - Embedded systems & hardware stuff

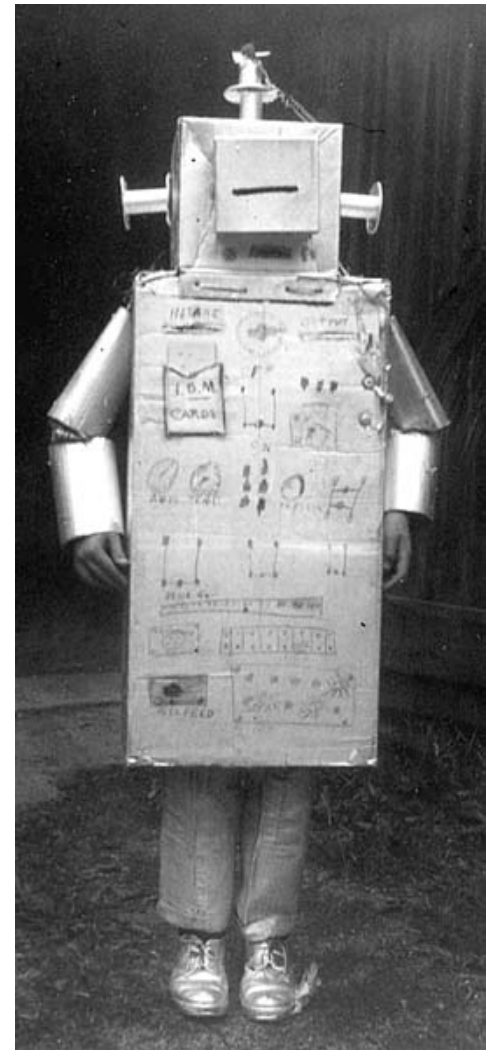

Sept 62