

Arduino Survival Guide Workshop Edition

~
Helping Your Arduino
Survive *You*

Ed Nisley • KE4ZNU
ed.nisley@pobox.com
softsolder.com

~
CNC Workshop
TechShop Detroit
June 2015



Bring This Stuff With You


- ♦ Laptop (with **Arduino board** + USB cable!)
 - ♦ **Arduino IDE** installed & tested
- ♦ **Digital Multimeter**
 - ♦ Volt • Amp • Ohm (optional: Freq • Diode • Cap • Induct)
 - ♦ Two (or more!) meters = better
- ♦ **Scientific Calculator** ($\sqrt{}$ power log **engineering**)
- ♦ **Power strip** / short extension cord
- ♦ Useful, but not absolutely essential
 - ♦ **Solderless breadboard** / **ProtoScrewShield**
 - ♦ **Soldering iron** & suchlike

The Big Picture

- **Arduino** stuff
 - It's a PCB with known pin layout & spacing
 - Atmel Atmega168 / 328 μ C + USB Interface
 - Power Source: USB or DC wall wart
 - Digital & analog I/O pins
- **Your** stuff
 - Draws power (ideally 5 V, maybe 12 V, or ...)
 - Connects to μ C I/O pins (5 V only!)
 - **Must** play well with Arduino

The Fundamental Units

 
- E = voltage: **volt V**
 - Millivolt $1 \text{ mV} = 0.001 \text{ V}$
- I = current: **ampere A**
 - **Milliampere $1 \text{ mA} = 0.001 \text{ A}$**
- R = resistance: **ohm Ω**
 - **Kilohm $1 \text{ k}\Omega = 1000 \Omega$**



Current

Lab: Measure Resistor Circuit

 - ♦ Set meter to Ω = ohms
 - ♦ Measure **resistance**
- ♦ Set meter to V = volts
 - ♦ Measure **voltage**
- ♦ Set meter to A = amps
 - ♦ (Re-plug leads?)
 - ♦ Measure **current**
 - ♦ (Re-plug leads?)



One Rule To Bind Them All

- ♦ Ohm's Law
 - ♦ $I = E / R$ (know R, measure E, get current!)
 - ♦ $E = I \cdot R$
 - ♦ $R = E / I$
- ♦ Most useful with resistors = known resistance
- ♦ You need a calculator and a multimeter ... *now!*

Lab: Verify Ohm's Law

- Using your measured values
 - Does measured **voltage** = (current x resistance)?
 - Does measured **current** = (voltage / resistance)?
 - Does measured **resistance** = (voltage / current)?
- How close did you come?
 - Percentage vs. absolute error
- What are the most accurate measurements?

The Power Rule


- ▶ Power dissipated in *resistors*
 - ▶ $P = I^2 \cdot R$
 - ▶ $P = E^2 / R$
 - ▶ You know R, so just measure E across resistor
- ▶ Power dissipated in *anything*
 - ▶ $P = E \cdot I$
 - ▶ If there's an R in series, measure E to find I...
- ▶ P = power: W watt
 - ▶ Milliwatt 1 mW = 0.001 W

Lab: Calculate Power

- ▶ Using your measured values
- ▶ Calculate power dissipated in resistor
 - ▶ Power = voltage x current
 - ▶ Power = voltage² / resistance
 - ▶ Power = current² x resistance
- ▶ How close are those three values?
 - ▶ Percentage vs. absolute error


Capacitance

 - ◆ C = capacitance: farad F
 - ◆ Millifarad
 - ◆ $1 \text{ mF} = 0.001 \text{ F} = 10^{-3} \text{ F}$
 - ◆ Microfarad
 - ◆ $1 \mu\text{F} = 0.000\,001 \text{ F} = 10^{-6} \text{ F}$
 - ◆ Nanofarad
 - ◆ $1 \text{ nF} = 0.000\,000\,001 \text{ F} = 10^{-9} \text{ F}$
 - ◆ Picofarad
 - ◆ $1 \text{ pF} = 0.000\,000\,000\,001 \text{ F} = 10^{-12} \text{ F}$




Circuit Construction

 - ♦ Use a solid breadboard
- ♦ If it *can* move, *stop it...*
- ♦ Good connections FTW!
 - ♦ Power
 - ♦ Ground
 - ♦ Signal
- ♦ Build it right the first time
 - ♦ Or do it over and over ...
- ♦ Current > 1 A = think hard!




Power Supply

 - USB Supply $\neq 5.0\text{ V}$
 - Measure actual voltage!
 - Draw $< 200\text{ mA}$ from port
 - Max $\approx 500\text{ mA}$, usually
- Wall Wart $V_{\text{EXT}} \leq 12\text{ V}$
 - Loose wire? μC dies $> 5\text{ V}$!
 - Less heat @ $V_{\text{EXT}} = 9\text{ V}$
 - Keep regulator $<< 500\text{ mW}$
 - Power $P = (V_{\text{EXT}} - 5) * I$



Ground (a.k.a. Common)

 
- ♦ Reference = 0 V
- ♦ Sum of all currents
- ♦ AC + DC Signals
- ♦ Difficult to get right
 - ♦ High current = trouble
- ♦ Vital for good signals
 - ♦ Glitches & intermittents
- ♦ Impossible to fix later
 - ♦ Daisy chain = death



MOSFET $R_{DS(on)}$ Tester
PCB has **four** ground planes


Lab: Arduino Supply Voltages

 - ♦ Meter (-) terminal to GND pin
 - ♦ Measure V_{in} (from supply)
 - ♦ Measure $5V$ (= “5V”)
 - ♦ Measure $3.3V$ (= “3.3V”)
- ♦ If using external supply...
 - ♦ Measure V_{EXT} at source




Lab: Arduino Supply Current

 - Measure current from supply
 - USB needs inline tap
 - Wall wart can be cut & spliced
 - Cheap USB inline volt/ammeter




Lab: Calculate Arduino Power

 - ◆ Total power
 - ◆ “ V_{in} ” x supply current
- ◆ Regulator power
 - ◆ (“ V_{in} ” – “5V”) x supply current
 - ◆ Is it < 500 mW?
- ◆ Board power
 - ◆ “5V” x supply current
- ◆ Compare all those powers






Digital Input Pins

 - ♦ All pins are inputs before setup ()
 - ♦ `pinMode(2, INPUT)`
- ♦ Enable internal pullup resistors (always?)
 - ♦ `pinMode(2, INPUT_PULLUP)`
 - ♦ `digitalWrite(2, HIGH)`
- ♦ *Do not* depend on pullup resistor value
 - ♦ Min 20 k Ω – what everyone assumes it is
 - ♦ Max 50 k Ω – what it might actually be
- ♦ `digitalRead(2)`




Lab: Measure Arduino Pullup

 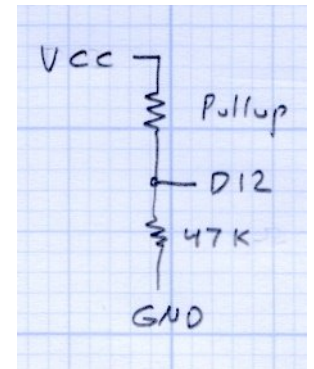 - Insert 47 kΩ resistor: D12 - GND
- `pinMode(12, INPUT_PULLUP)`
 - Modify Blink example!
- Measure V across resistor
- Compute:
 - Current through resistor: $I = E / R$
 - Voltage across pullup: “5V” - V
 - Pullup resistance
 - Know voltage & current: $R = E / I$
- Is pullup $\geq 20 \text{ k}\Omega$ and $\leq 50 \text{ k}\Omega$?




Digital Output Pins

 - ◆ Configure pins for output in `setup()`
 - ◆ `pinMode(2, OUTPUT)`
- ◆ Outputs HIGH = 5 V or LOW = 0 V
 - ◆ Depends on load: measure!
- ◆ Current ≤ 40 mA / pin = *absolute max*
 - ◆ Happiness $\uparrow\uparrow$ for current ≤ 20 mA
 - ◆ Enough for one standard LED...
- ◆ Maximum **total** μC current ≤ 200 mA
 - ◆ Draw *much* less than that: ≤ 100 mA max




Additional Digital I/O Pins!

 - ◆ Reconfigure **Analog Input** pins
 - ◆ `pinMode(A0, INPUT_PULLUP)`
 - ◆ `pinMode(A0, OUTPUT)`
- ◆ The usual digital functions
 - ◆ `digitalWrite(A0, LOW)`
 - ◆ `digitalRead(A0)`
- ◆ No analog *output*
 - ◆ ~~`analogWrite(A0, 128)`~~





Switch Inputs

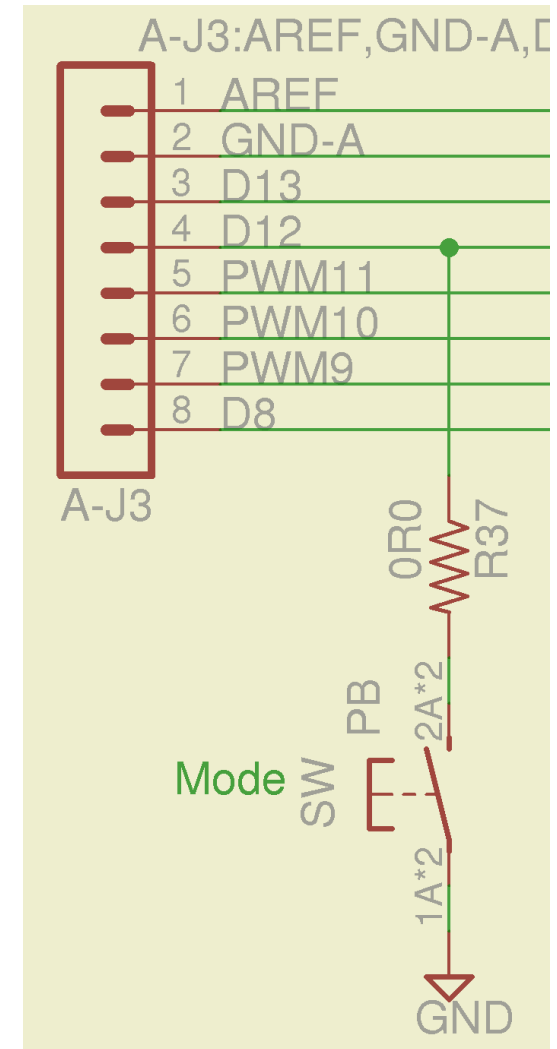- Connect input pin to ground
 - This **kills output** pins = HIGH
 - Add 1 k Ω series R for protection?
- Enable internal pullup
 - `pinMode(12, INPUT_PULLUP)`
- Add external pullup \approx 10 k Ω
- Pin states track *voltages*
 - Closed** = pushed = LOW = **false**
 - Open** = released = HIGH = **true**




Switch Contact Bounce

  - ◆ Glitches galore!
 - ◆ Time scale = 10 ms/div
 - ◆ Unpredictable events
- ◆ Add parallel C = **bad**
 - ◆ Resonant with stray L
 - ◆ Voltage spikes!
- ◆ Use e.g. **Bounce** library
 - ◆ **Don't** roll your own
- ◆ Plan for the worst case




Lab: Measure Contact Bounce

 - Use a grotty switch!
- `pinMode(2, INPUT_PULLUP)`
- Loop 1 second while testing D2
 - Hint: `millis() + 1000`
 - Hint: `D2 != previous value?`
 - Count each change
- Print/clear total every second
- Bonus
 - External Interrupt on D2 edge
 - Pin-change interrupt




“Analog” Output

 - ♦ It's not *analog*, it's *digital* ...
 - ♦ PWM = P **u**lse W **i**dth M **o**dulation
 - ♦ Output pins 3, 5, 6, 9, 10, 11 *only*
- ♦ `analogWrite(3, 100)`
 - ♦ Minimum = 0 → 0 V (steady, per load)
 - ♦ Maximum = 255 → 5 V (steady, per load)
 - ♦ $0 < \text{“analog PWM”} < 255 \rightarrow \text{pulses (duh)}$
- ♦ PWM frequency ≈ 488 & 976 Hz
 - ♦ Direct LED drive works fine




Real Analog Output

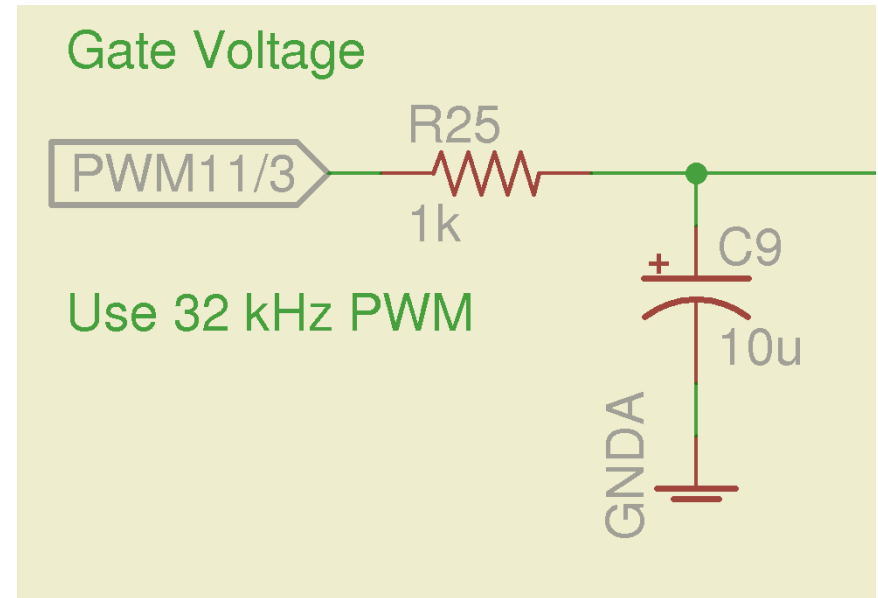- ◆ Filter PWM → Analog
 - ◆ Simple RC filter OK
 - ◆ $R \cdot C \gg 1/(2\pi \cdot \text{PWM freq})$
 - ◆ C can become nasty big
 - ◆ $\uparrow\uparrow \text{ PWM freq} = \downarrow\downarrow C$
- ◆ Analog buffer / op amp
 - ◆ Minimal load = good
 - ◆ Voltage scaling
- ◆ Wall wart = stable V (*duh*)




Analog Input

 - ♦ `analogRead(A0)`
 - ♦ Minimum 0 = 0V
 - ♦ Maximum 1023 = “5V” (pretty close)
 - ♦ Depends on **actual** supply voltage!
 - ♦ $\text{Value} = 1023 * (V / \text{AREF})$
- ♦ Wall wart = stable AREF = (*duh*)
- ♦ $0 \text{ V} \leq [\text{Analog voltage}] \leq 5 \text{ V}$
- ♦ Avoid digital pin output before AI
- ♦ Average several AI readings?




Single LED

 - ♦ Assume 20 mA max
 - ♦ *Continuous*, not *peak*
 - ♦ 10 mA = bright enough
 - ♦ Do you **know** different?
- ♦ Forward voltage drop
 - ♦ Red - orange = 2 V
 - ♦ Yellow - green = 2.5 V
 - ♦ Blue & white = 3.5 V
- ♦ Arduino = **one** LED / pin
 - ♦ Pin = 5 V & 20 mA **maximum**




https://en.wikipedia.org/wiki/LED_circuit

LED Forward Voltage vs. Color

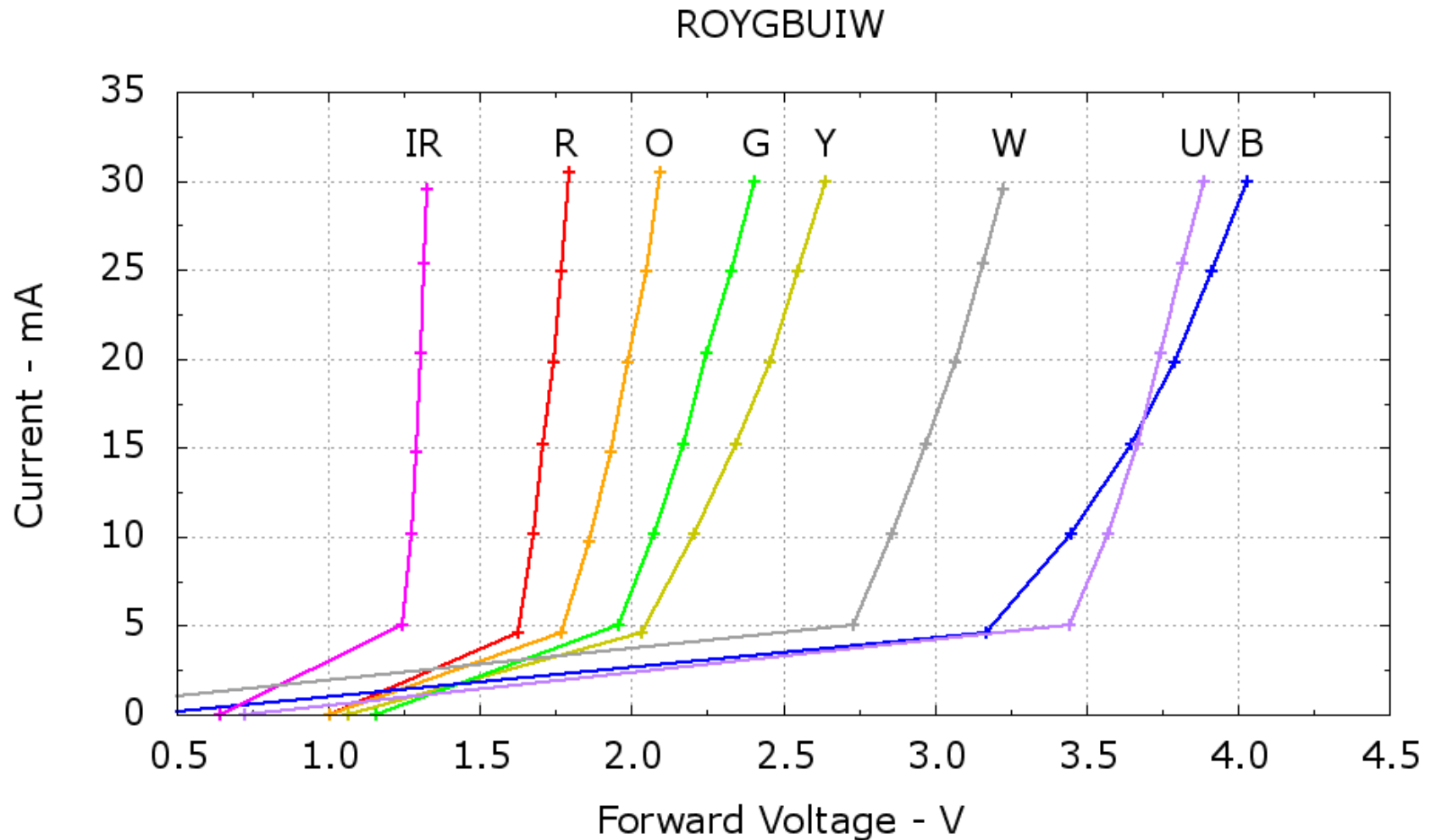


Single LED Resistor

- ▶ Resistor limits LED current
 - ▶ This is **not** optional!
- ▶ Ohm's Law **for resistor**: $R = V_R / I$
 - ▶ Want current $I = 10 \text{ mA}$ ($< 20 \text{ mA}$, OK?)
 - ▶ Same as LED because they're in series
 - ▶ Voltage = $V_{CC} - V_{LED} = "5V" - 1.8 \text{ V} = 3.2 \text{ V}$
 - ▶ V_{LED} **varies with color**, **so be careful**!
 - ▶ Resistance = $R = V / I = 3.2 / 0.01 = 320 \Omega$
 - ▶ Round **up** to next standard value = 330Ω
- ▶ **Measure** actual V_R to verify: $I = V_R / R$

 


Lab: Measure LED Voltage

 - ▶ LED
 - ▶ Pick a color
 - ▶ Use $R = 270\ \Omega$? (compute current)
- ▶ Program
 - ▶ `pinMode(11, OUTPUT)`
 - ▶ `digitalWrite(11, HIGH)`
 - ▶ `Print analogRead(A0)`
 - ▶ Compute actual voltage
- ▶ Bonus
 - ▶ Compute LED current
 - ▶ Compute LED power




LED Strips & Rings

 - ♦ 3 LEDs + R / section
 - ♦ $I = 20 \text{ mA}$ typical
 - ♦ $V = 12 \text{ V}$ supply
 - ♦ Sections in parallel
- ♦ **Cannot** use μC pin (!)
 - ♦ MOSFET driver?
- ♦ RGB LEDs = 3 strings
 - ♦ Different resistors!
 - ♦ Measure V_R to find I



LED Strip Driver

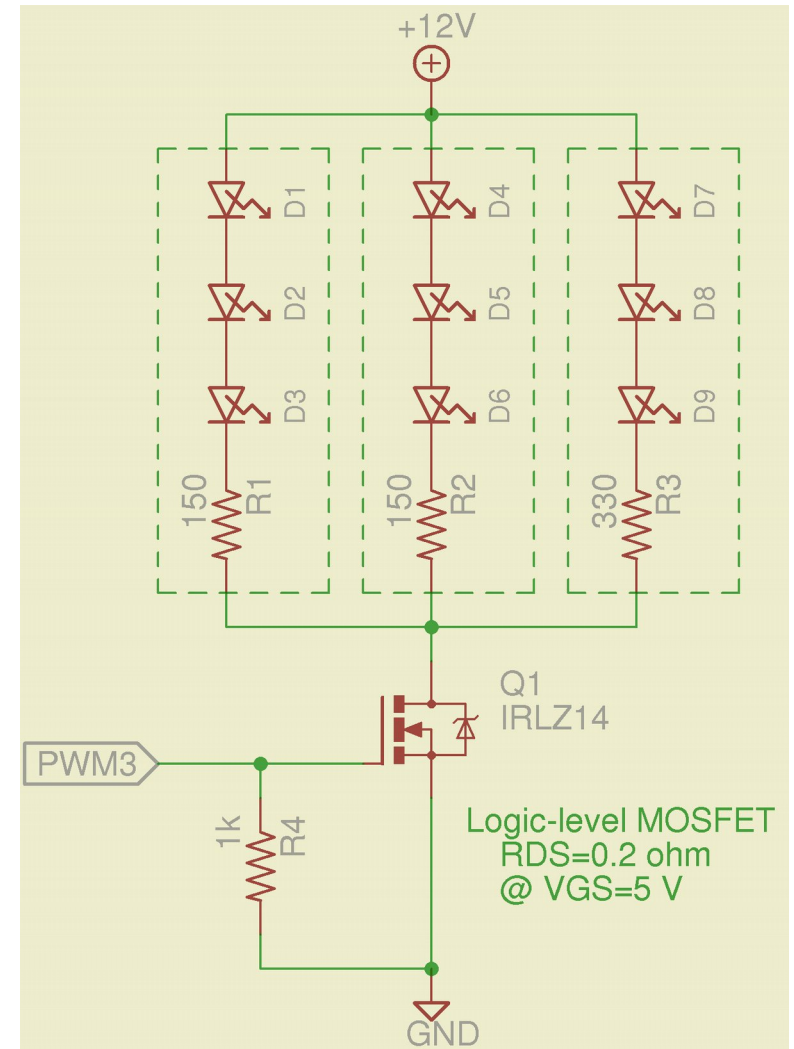- ▶ 3 LED sections = 60 mA
- ▶ Logic-level MOSFET
- ▶ Must have gate pulldown R
 - ▶ Override μC internal pullup
- ▶ More sections = heatsink!
 - ▶ MOSFET $P = I^2 \cdot R_{\text{DS}}$
- ▶ May need RC snubber
 - ▶ Stray inductance (!)



Other Gotchas

- ♦ Motors
 - ♦ DC – H-bridge driver
 - ♦ Steppers – microstep
 - ♦ Servo – PWM
- ♦ Noisemakers
 - ♦ Piezo
 - ♦ Speaker
- ♦ Keyboard / Keypads
- ♦ Thermistors
- ♦ SPI / I²C / OWP chips
- ♦ LCD Panels
- ♦ LED Char / Dot Matrix
- ♦ EEPROM / SD Data
- ♦ Ethernet / WiFi
- ♦ Zigbee / XBee
- ♦ Accelerometers
- ♦ ...

Everything Else

Is

A Simple Matter of Software

More Info

arduino.cc/en/Reference/HomePage
www.ladyada.net/learn/arduino/index.html
todbot.com/blog/spookyarduino/
www.sparkfun.com/tutorials

and, of course ...
softsolder.com/tag/arduino/

Copyright-ish Stuff

Some web images probably copyrighted, but
shown & attributed here under “fair use”
[whatever that is]

The rest is my own work



This work is licensed under the
Creative Commons Attribution-Noncommercial-Share Alike 3.0 United States License.

To view a copy of this license, visit

<http://creativecommons.org/licenses/by-nc-sa/3.0/us/>

or send a letter to

Creative Commons, 543 Howard Street, 5th Floor
San Francisco, California, 94105, USA.



Ed Nisley

Say “NISS-lee”, although we're on the half-essed branch of the tree

Engineer (ex PE), Hardware Hacker, Programmer, Author

[The Embedded PC's ISA Bus: Firmware, Gadgets, Practical Tricks](#)

Circuit Cellar www.circuitcellar.com

Firmware Furnace (1988-1996) - Nasty, grubby hardware bashing

Above the Ground Plane (2001 ...) - Analog and RF stuff

Digital Machinist www.homeshopmachinist.net


Along the G-Code Way (2008 ...) - G-Code, math, 3D printing

Dr. Dobb's Journal www.ddj.com

Embedded Space (2001-2006) - All things embedded

Nisley's Notebook (2006-2007) - Hardware & software collisions

My Blog: The Smell of Molten Projects in the Morning
softsolder.com

 

September 1962



If you
can't read this
then
make a new friend
'way up front